

ECE 443 APPLIED ELECTRONICS - LAB 10 CRYSTAL OSCILLATOR

G. Sener

Cankaya University, Electronics and Communication Engineering
Department,
06810, Yenimahalle, Ankara, Turkey.
email: sener@cankaya.edu.tr

Abstract—This lab experiment aims to teach students how to implement the rf crystal oscillator.

1. METHODS

Parts: $R = 10k\Omega$, $C = 47pF$, $Q = BD137$ bjt transistor

1. Implement the following circuit (Fig.1).
2. Observe the amplitude of the output waveform and draw it in your

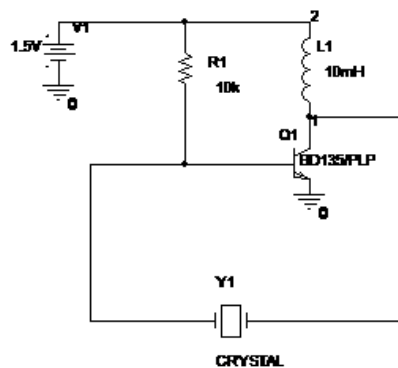


Figure 1. a)Circuit Diagram

lab notebook.

3. Comment on the results.

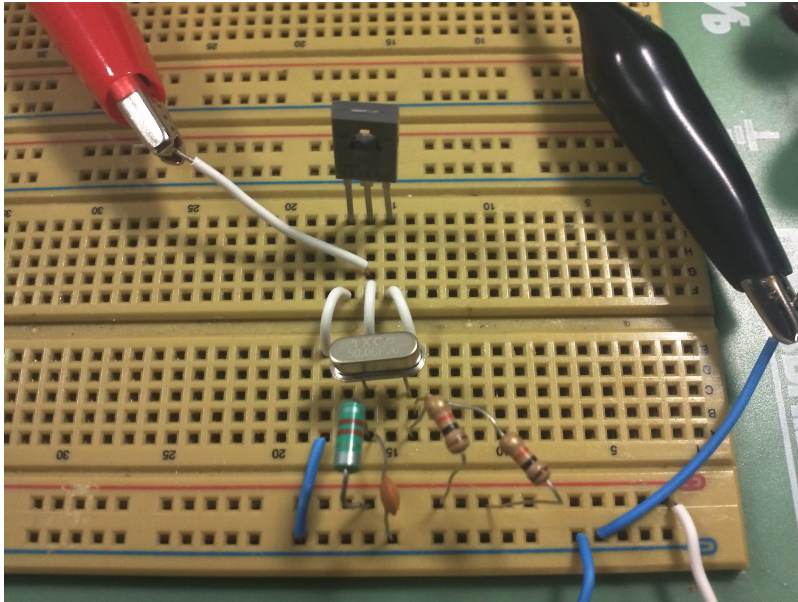


Figure 2. a)PCB Circuit Diagram

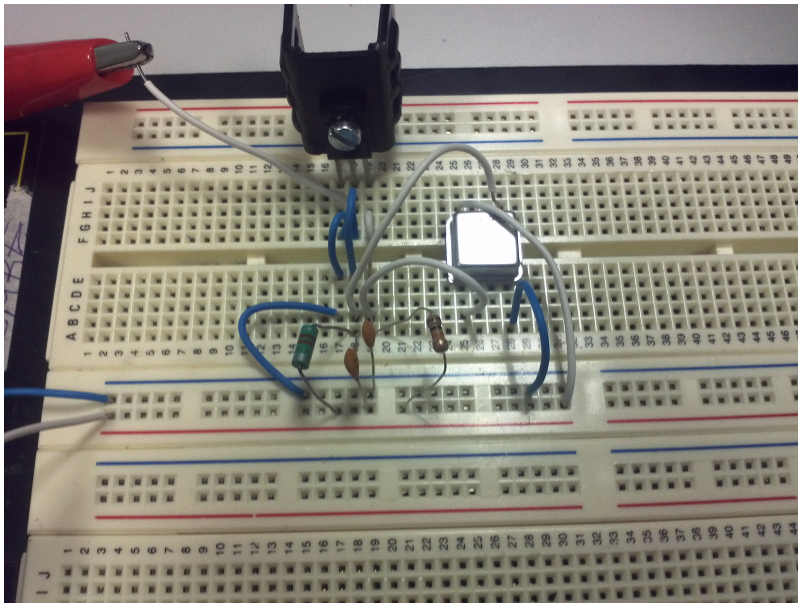


Figure 3. a)PCB Circuit Diagram