

ECE 443 APPLIED ELECTRONICS - LAB 2 FREQUENCY RESPONSE

G. Sener

Cankaya University, Electronics and Communication Engineering
Department,
06810, Yenimahalle, Ankara, Turkey.
email: sener@cankaya.edu.tr

Abstract—This lab experiment aims to teach students the effect of frequency on the operation of linear circuits such as the amplifier.

1. METHODS

Parts: BD135 or BD137 bjt transistor, $R=100k$, $R=600$, $C=0.1\mu F$ (2x)
caps. 1. Connect the following circuit (Fig.1a).

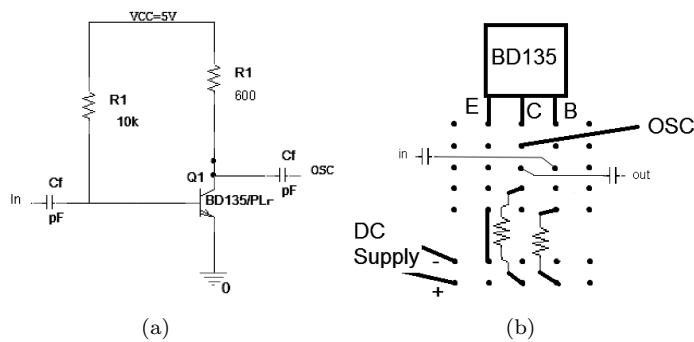


Figure 1. a) Circuit Diagram, b) Circuit layout

2. For V_{in} amplitude of 20mV, Increase the input frequency ($f=1kHz, 100kHz, 1,2,3,4,5,6,7,8,9,10$ MHz) and record the output amplitude values. Draw the Gain vs. frequency graph. Make a conclusion. Note: $Gain = v_{out}(pk-pk)/v_{in}(pk-pk)$.